

*ELEC0029 - Electric power systems analysis and operation*

## Analysis of balanced faults


Thierry Van Cutsem

[t.vancutsem@ulg.ac.be](mailto:t.vancutsem@ulg.ac.be)


[www.montefiore.ulg.ac.be/~vct](http://www.montefiore.ulg.ac.be/~vct)

March 2020


# Types of faults

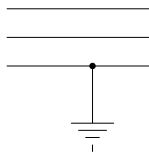


single phase to ground  
*monophasé*

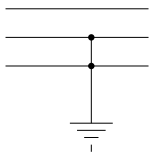

double phase to ground  
*biphasé terre*

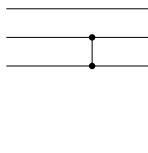

phase to phase  
*biphasé*

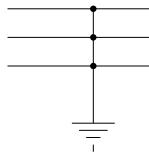

three-phase  
*triphasé*

Single phase to ground faults :

- the most frequent.

Example : Belgian 400-kV grid : 91 % of faults (2006-2014)

Three-phase faults :

- much less frequent. Example : Belgian 400-kV grid : only 2 % of faults
- but very often the most severe
- worst case that the network must be able to withstand.

This chapter focuses on three-phase faults with the same (in particular zero) resistance between each phase and the ground


- the network remains electrically balanced → *balanced fault analysis*
- per-phase analysis can still be used.

# Behaviour of the synchronous machine during a three-phase fault

Please refer to the separate lecture:

*Behaviour of synchronous machine during a short-circuit  
(a simple example of electromagnetic transients)*

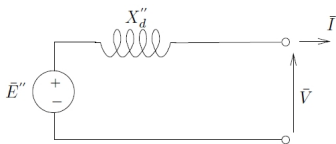where the equivalent circuit of the machine is derived:



The stator resistance being small, it is usually neglected in short-circuit calculations

# Computation of three-phase short-circuit currents

## Motivation

- dimensioning the circuit breakers: breaking capability must be sufficient
- adjusting the settings of protections:
  - must not act in normal operation
  - must act in case of a fault.


## Assumptions

- network with  $N$  nodes
- $n$  synchronous machines connected to nodes 1 to  $n$  (for simplicity)
- each synchronous machine represented by its equivalent circuit ( $\bar{E}''$ ,  $X''$ ) (stator resistance neglected)
- loads represented by constant (shunt) admittances, obtained from the pre-fault operating conditions:


$$Y_c = \frac{P^{pre} - jQ^{pre}}{[V^{pre}]^2}$$

- node  $f$  subject to a short-circuit with impedance  $Z_f$ .

## machines with Thévenin equivalents

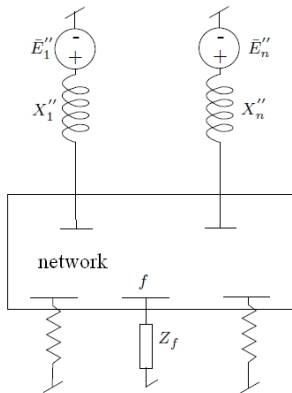

## machines with Norton equivalents

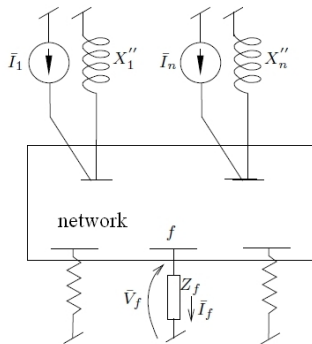


$$\bar{I} = \mathbf{Y} \bar{V}$$

$\bar{I}$  : vector of complex currents injected in the  $N$  buses,  
each current counted positive if it enters the network


$\bar{V}$  : vector of complex voltages at the  $N$  buses

$\mathbf{Y}$  : bus (or nodal) admittance matrix
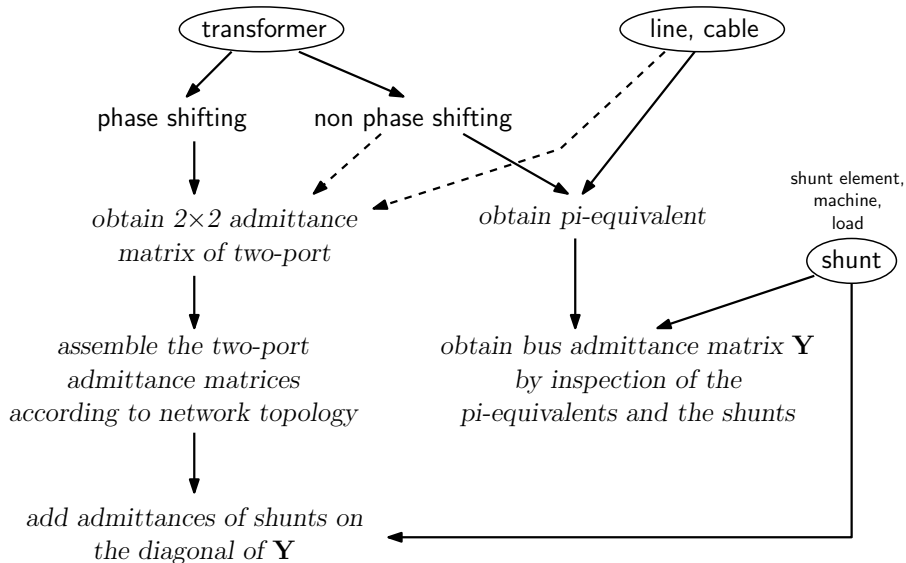
# Determination of the bus (or nodal) admittance matrix


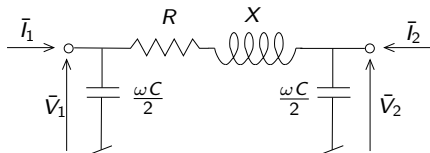
## Admittance matrix of the two-port representing a line or a cable




$$\bar{I}_1 = j\frac{\omega C}{2}\bar{V}_1 + \frac{1}{R+jX}(\bar{V}_1 - \bar{V}_2) = \left(j\frac{\omega C}{2} + \frac{1}{R+jX}\right)\bar{V}_1 - \frac{1}{R+jX}\bar{V}_2$$

$$\bar{I}_2 = j\frac{\omega C}{2}\bar{V}_2 + \frac{1}{R+jX}(\bar{V}_2 - \bar{V}_1) = -\frac{1}{R+jX}\bar{V}_1 + \left(j\frac{\omega C}{2} + \frac{1}{R+jX}\right)\bar{V}_2$$

and hence:

$$\mathbf{Y} = \begin{bmatrix} j\frac{\omega C}{2} + \frac{1}{R+jX} & -\frac{1}{R+jX} \\ -\frac{1}{R+jX} & j\frac{\omega C}{2} + \frac{1}{R+jX} \end{bmatrix}$$
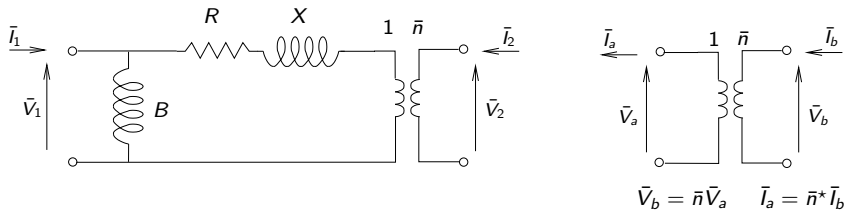
## Admittance matrix of the two-port representing a transformer (including the case of a phase shifter)



$$\bar{I}_1 = jB\bar{V}_1 + \frac{1}{R+jX}(\bar{V}_1 - \frac{\bar{V}_2}{\bar{n}}) = (jB + \frac{1}{R+jX})\bar{V}_1 - \frac{1}{(R+jX)\bar{n}}\bar{V}_2$$

$$\bar{I}_2 = \frac{1}{\bar{n}^*}(\frac{\bar{V}_2}{\bar{n}} - \bar{V}_1)\frac{1}{R+jX} = -\frac{1}{(R+jX)\bar{n}^*}\bar{V}_1 + \frac{1}{(R+jX)\bar{n}^2}\bar{V}_2$$

and hence:

$$\mathbf{Y} = \begin{bmatrix} jB + \frac{1}{R+jX} & -\frac{1}{(R+jX)\bar{n}} \\ -\frac{1}{(R+jX)\bar{n}^*} & \frac{1}{(R+jX)\bar{n}^2} \end{bmatrix}$$

non symmetric if the transformer ratio is a complex number (phase shifter)




## Assembling the two-port admittance matrices according to topology

For an  $N$ -bus system:

- initialize  $\mathbf{Y}$  to a zero matrix of dimensions  $N \times N$
- determine the  $(2 \times 2)$  admittance matrices of the two-ports representing the lines, the cables and the transformers
- add the four terms of each of those matrices to the proper terms of  $\mathbf{Y}$ , taking into account the numbering of the terminal nodes
- add the admittances of machines, loads and shunt compensation elements to the corresponding diagonal terms of  $\mathbf{Y}$ .


## Example on a four-bus network

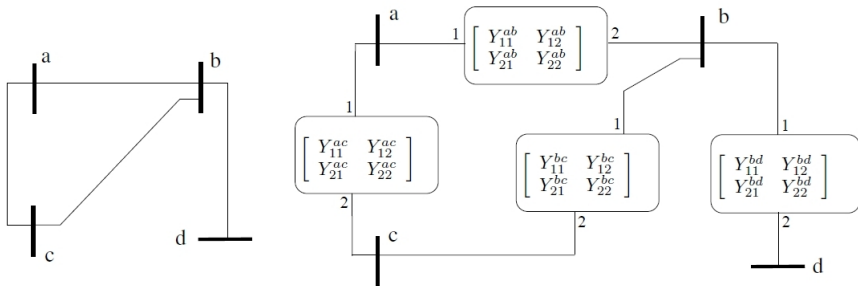

$$\mathbf{Y} = \begin{bmatrix} Y_{11}^{ab} + Y_{11}^{ac} & Y_{12}^{ab} & Y_{12}^{ac} & 0 \\ Y_{21}^{ab} & Y_{22}^{ab} + Y_{11}^{bc} + Y_{11}^{bd} & Y_{12}^{bc} & Y_{12}^{bd} \\ Y_{21}^{ac} & Y_{21}^{bc} & Y_{22}^{ac} + Y_{22}^{bc} & 0 \\ 0 & Y_{21}^{bd} & 0 & Y_{22}^{bd} \end{bmatrix}$$
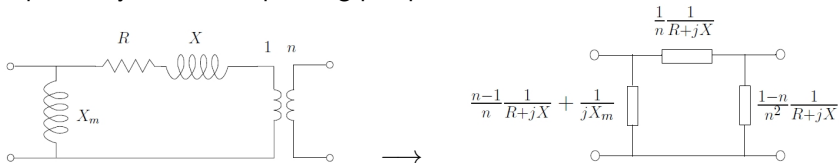
## Method by inspection

- Lines and cables are represented by their pi-equivalents
- the equivalent circuits of transformers *without phase shift* (real ratio  $n$ ) are replaced by their corresponding pi-equivalents:



- those pi-equivalents are assembled according to the network topology
- together with the admittances of shunts
- the terms of  $\mathbf{Y}$  are determined *by inspection* as follows:
  - the off-diagonal term  $[\mathbf{Y}]_{ij}$  ( $i, j = 1, \dots, N; i \neq j$ ) is the sum of the admittances of all the elements connecting nodes  $i$  and  $j$ , sign changed
  - the diagonal term  $[\mathbf{Y}]_{ii}$  ( $i = 1, \dots, N$ ) is the sum of the admittances of all the elements connected to node  $i$ .

**Exercise.** Use the method by inspection to check that the transformer pi-equivalent shown above has the  $(2 \times 2)$  admittance matrix given in slide #8.

# Computation of during-fault voltages by superposition

From the during-fault voltages, the current in any component can be computed.

The fault admittance  $Y_f = \frac{1}{Z_f}$  is **not included** in  $\mathbf{Y}$ . Indeed:

- many possible fault locations have to be analyzed.  
Including  $Y_f$  in  $\mathbf{Y}$  would require modifying  $\mathbf{Y}$  for each fault location
- “solid” faults are considered (as worst cases):  $Z_f = 0 \Rightarrow Y_f \rightarrow \infty$   
cannot be included in  $\mathbf{Y}$  !

The derivation which follows:

- uses the  $\mathbf{Y}$  matrix relative to the **pre-fault** configuration of the network
- encompasses the case  $Z_f = 0$ .

Under the combined effect of  $(\bar{I}_1, \bar{I}_2, \dots, \bar{I}_n)$  and  $\bar{I}_f$ , the voltages  $\bar{V}$  are such that:

$$Y \bar{V} = \begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \\ \vdots \\ \bar{I}_n \\ 0 \\ \vdots \\ \vdots \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ \vdots \\ \vdots \\ 0 \\ -\bar{I}_f \\ 0 \\ \vdots \\ 0 \end{bmatrix}$$

By superposition :

$$\bar{\mathbf{V}} = \bar{\mathbf{V}}^{pre} + \Delta\bar{\mathbf{V}} \quad (1)$$

with:

$$\mathbf{Y} \bar{\mathbf{V}}^{pre} = \begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \\ \vdots \\ \bar{I}_n \\ 0 \\ \vdots \\ \vdots \\ 0 \end{bmatrix} \quad \text{and} \quad \mathbf{Y} \Delta\bar{\mathbf{V}} = -\bar{I}_f \begin{bmatrix} 0 \\ \vdots \\ \vdots \\ 0 \\ 1 \\ 0 \\ \vdots \\ 0 \end{bmatrix} = -\bar{I}_f \mathbf{e}_f$$

$\bar{\mathbf{V}}^{pre}$  : vector of pre-fault bus voltages

$\Delta\bar{\mathbf{V}}$  : correction accounting for the short-circuit

$\mathbf{e}_f$  : unit vector (all zero components, except the  $f$ -th one equal to 1).

At this step, the value of  $\bar{I}_f$  is still unknown. . .

Let us solve provisionally:

$$\mathbf{Y} \Delta \bar{\mathbf{V}}^1 = \mathbf{e}_f$$

We have:

$$\Delta \bar{\mathbf{V}} = -\bar{\mathbf{I}}_f \Delta \bar{\mathbf{V}}^1$$

Introducing this result in (1):

$$\bar{\mathbf{V}} = \bar{\mathbf{V}}^{pre} - \bar{\mathbf{I}}_f \Delta \bar{\mathbf{V}}^1$$

The  $f$ -th component of this relation is:

$$\bar{V}_f = \bar{V}_f^{pre} - \bar{I}_f \Delta \bar{V}_f^1$$


Combining with  $\bar{V}_f = Z_f \bar{I}_f$  we obtain:

$$\bar{I}_f = \frac{\bar{V}_f^{pre}}{\Delta \bar{V}_f^1 + Z_f} \quad (2)$$

Substituting in (1), the during fault voltages are given by:

$$\bar{\mathbf{V}} = \bar{\mathbf{V}}^{pre} - \frac{\bar{V}_f^{pre}}{\Delta \bar{V}_f^1 + Z_f} \Delta \bar{\mathbf{V}}^1$$

# Relation with Thévenin equivalent

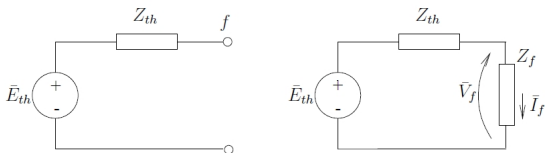

Thévenin equivalent seen from node  $f$ :

- emf:  $\bar{E}_{th} = \bar{V}_f^{pre}$
- impedance:  $Z_{th}$  = voltage at node  $f$  when a unit current is injected in this node, after the other current injectors have been replaced by open-circuits.

Thus:

$$Z_{th} = [\mathbf{Y}^{-1} \mathbf{e}_f]_f = [\Delta \bar{\mathbf{V}}^1]_f = \Delta \bar{V}_f^1$$

Fault current: 
$$\bar{I}_f = \frac{\bar{E}_{th}}{Z_{th} + Z_f} = \frac{\bar{V}_f^{pre}}{\Delta \bar{V}_f^1 + Z_f} \quad \text{which is nothing but Eq. (2)}$$

Another way to obtain  $Z_{th}$ : 
$$Z_{th} = [\mathbf{Y}^{-1} \mathbf{e}_f]_f = [\mathbf{Y}^{-1}]_{ff} = [\mathbf{Z}]_{ff}$$

$\mathbf{Z}$  is called the *nodal impedance matrix*